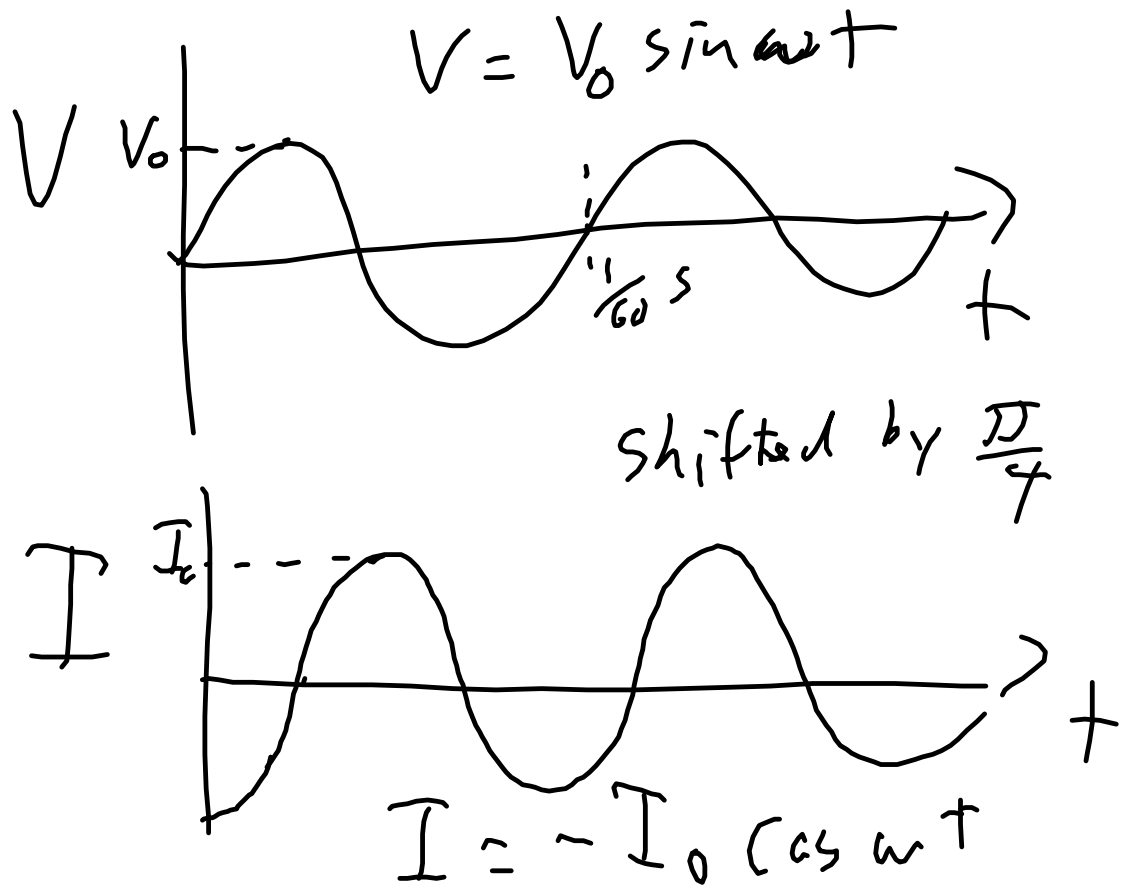


Recap AC, Kirchhoff's Laws, Internal Resistance

Alternating Current, AC




$$V_{rms} = \frac{V_0}{\sqrt{2}} \qquad I_{rms} = \frac{I_0}{\sqrt{2}}$$

↑ root mean square

$$P = VI$$

$$P = P_{\max} \sin^2 \omega t$$

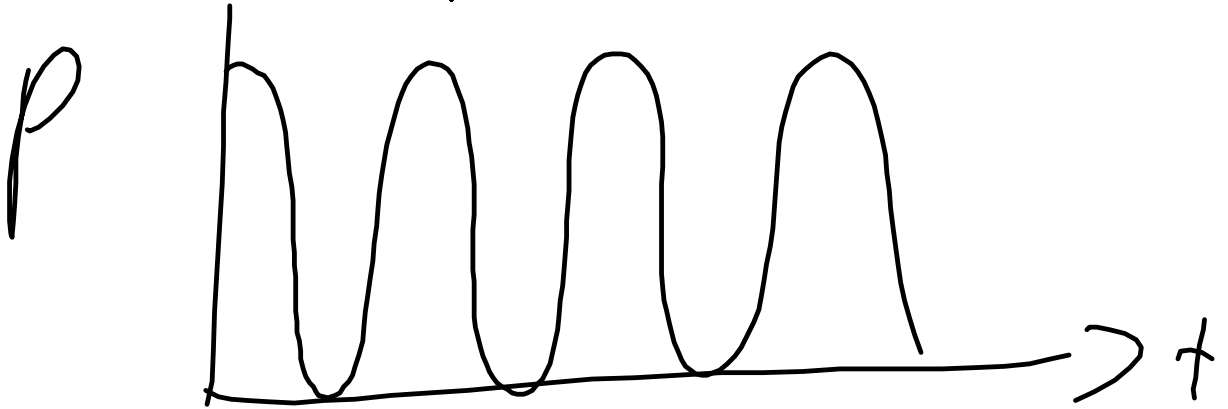


$$P_{\max} = V_0 I_0 \quad \xrightarrow{\text{avg}} \quad \bar{P} = V_{\text{rms}} \times I_{\text{rms}}$$

$$\bar{P} = \frac{V_0}{\sqrt{2}} \frac{I_0}{\sqrt{2}}$$

$$\bar{P} = \frac{V_0 I_0}{2} = \frac{P_{\max}}{2}$$

Kirchhoff's Laws

Loop law, KLL

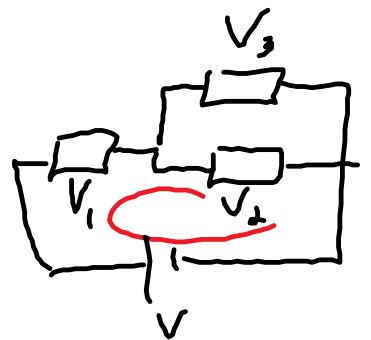


$$\sum V \text{ around a loop} = 0 \quad V_2 = V_3$$

$$V = V_1 + V_2$$




$$V = V_1 + V_3$$

junction Law, KJL

$$I_{in} = I_{out}$$

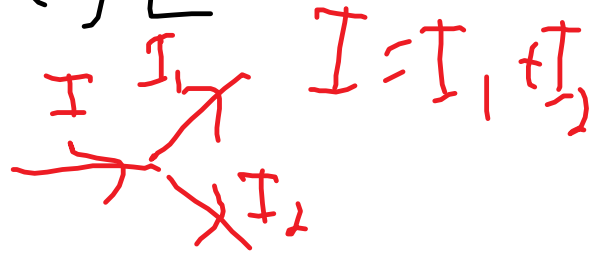

Symbols:

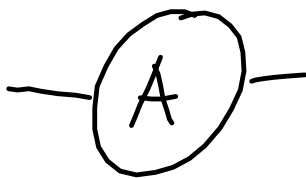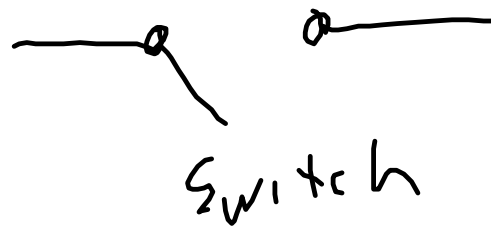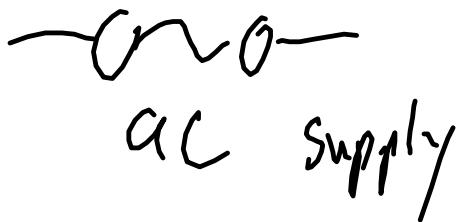

Ammeter



must be in
Series



Voltmeter



Put in Parallel

across element


1000 1000 1000 1000

Galvanometer



Galvanometer
- small
currents


Series
 - replaces a wire
 ideal $r = 0$

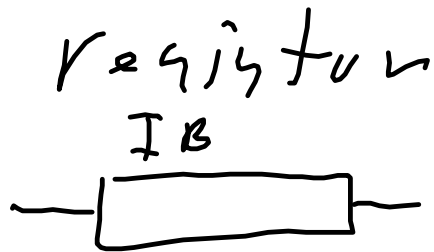


book




Lamp

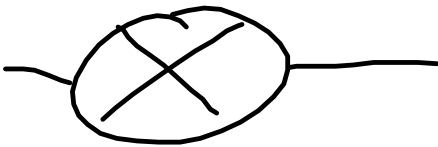

book

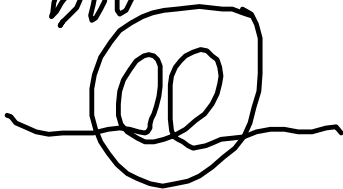


diode

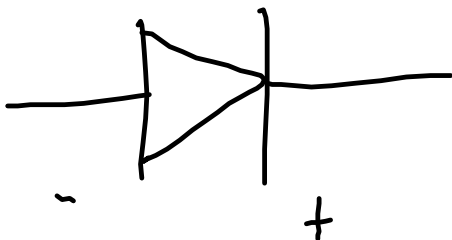


across element
 you are measuring
 ideal $r = \infty$


Variable resistor

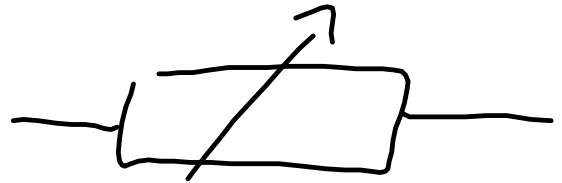


Potentiometer

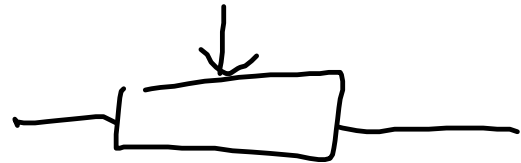

thermistor

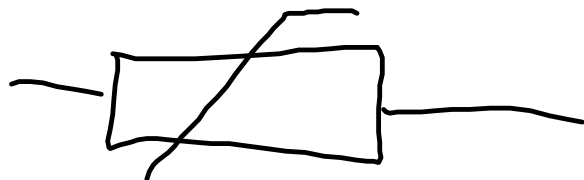


Capacitor

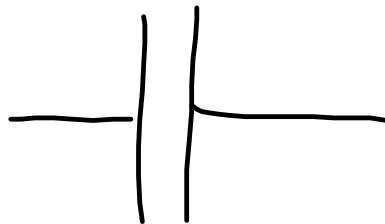

A 8.0v battery is connected to a 100 ohm resistor then the wire splits into a 75 ohm and 50 ohm resistor (in parallel to each other) and join up back to the battery.

- Draw the circuit diagram, showing the location of a voltmeter and ammeter to measure the properties of the 75 ohm resistor.
- What is the equivalent resistance?
- What is the current out of the battery?
- What are the values registered on the ammeter and voltmeter?
- Which resistor dissipates the most power?
- If the current through the 75 ohm resistor is only 13mA, determine the internal resistance of the battery.
- If a 6.0 V batter is placed in series with the 75ohm resistor reverse polarized (positive towards positive) - determine the current through the 50 ohm resistor. (ignore internal resistance)

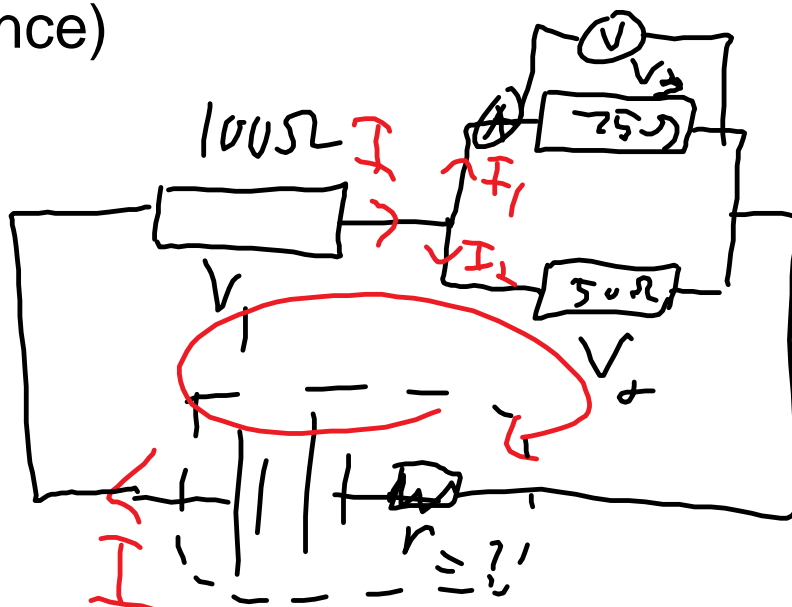

$$I = I_1 + I_2$$

$$V = V_1 + V_2$$

$$V = V_1 + V_3$$


$$V = 8.0V$$

Series

$$R_T = R_1 + R_2$$

$$P = P_1 + P_2 + P_3$$

Wheatstone Bridge

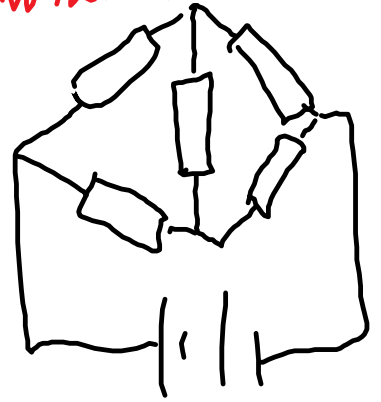

Parallel

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{Total}} = \frac{1}{50} + \frac{1}{75} = \frac{3}{150} + \frac{2}{150}$$

$$R_T = 30\Omega$$

$$R_T = 30\Omega + 100\Omega = 130\Omega$$

$$I = \frac{V}{R_T} = \frac{8.0V}{130\Omega} = \boxed{62mA}$$